

Digital Design with the Verilog HDL

Chapter 5 Behavioral Model - part 2

Binh Tran-Thanh

Department of Computer Engineering
Faculty of Computer Science and Engineering
Ho Chi Minh City University of Technology

May 26, 2023



Interacting Behaviors [1]

- Assignments can trigger other assignments
- Non-blocking assignments CAN trigger blocking assignments

```
always @(posedge clk) begin          always @(A, C) begin
    ...                               ...
    A <= B;                            D = A & C;
    ...                               ...
end                                    end
```

- In hardware, reflects that the output of the A flip flop or register can be the input to combinational logic
- When the FF changes value, that change must propagate through the combinational logic it feeds into



Interacting Behaviors [2]

```
always @(posedge clk or posedge rst) begin // behavior1
    if(rst) y1 = 0; //rst
    else y1 = y2;
end
```

```
always @(posedge clk or posedge rst) begin // behavior2
    if(rst) y2 = 1; // prst
    else y2 = y1;
end
```

- If behavior1 always first after rst, $y1 = y2 = 1$
- If behavior2 always first after rst, $y2 = y1 = 0$.
- Results are order dependent, ambiguous –race condition!
- This is why we don't use blocking assigns for flip-flops...



Interacting Behaviors [3]

```
always @(posedge clk or posedge rst) begin
    if(rst) y1 <= 0; //rst
    else y1 <= y2;
end
```

```
always @(posedge clk or posedge rst) begin
    if(rst) y2 <= 1; // prst
    else y2 <= y1;
end
```

- Assignments for y1 and y2 occur in **parallel**
- $y1 = 1$ and $y2 = 0$ after rst
- Values swap each clk cycle after the rst
- No race condition!



Synchronous/Asynchronous rst

- Synchronous: triggered by **clk** signal

```
module dff_sync(output reg Q,  
               input D, clk, rst);  
    always @(posedge clk) begin  
        if(rst) Q <= 1'b0;  
        else Q <= D;  
    end  
endmodule
```

- Asynchronous: also triggered by **rst** signal

```
module dff_async(output reg Q,  
                input D, clk, rst, en);  
    always @(posedge clk, posedge rst) begin  
        if(rst) Q <= 1'b0;  
        else if (en) Q <= D;  
    end  
endmodule
```



What Happens Here?

```
module dff_BAD(reg output Q,  
               input D, clk, rst);  
    always @(posedge clk, rst) begin  
        if(rst) Q <= 1'b0;  
        else Q <= D;  
    end  
endmodule
```

Does this give incorrect behavior?



Datatype Categories

Net

- Represents a physical wire
- Describes structural connectivity
- Assigned to in continuous assignment statements
- Outputs of primitives and instantiated sub-modules

Variables

- Used in Behavioral procedural blocks
- Can represent:
 - Synchronous registers
 - Combinational logic



Variable Datatypes

- **reg** –scalar or vector binary values
- **integer** –32 or more bits
- **time** –time values represented in 64 bits (unsigned)
- **real** –double real values in 64 or more bits
- **realtime** -stores time as double real (64-bit +)
- Assigned value only within a behavioral block
- CANNOT USE AS:
 - Output of primitive gate or instantiated submodule
 - LHS of continuous assignment
 - Input or inout port within a module
- **real** and **realtime** initialize to 0.0, others to x...
 - Just initialize yourself!



Examples Of Variables

```
reg signed [7:0] A_reg; // 8-bit signed vector register
reg Reg_Array [7:0]; // array of eight 1-bit registers
integer Int_Array [1:100]; // array of 100 integers
real B, Real_Array [0:5]; // scalar & array of 6 reals
time Time_Array [1:100]; // array of 100 times
real timeD, Real_Time [1:5]; // scalar & array of 5
    realtimes
initial begin
    A_reg = 8'ha6; // Assigns all eight bits
    Reg_Array[7] = 1; // Assigns one bit
    Int_Array[3] = -1; // Assign integer -1
    B = 1.23e-4; // Assign real
    Time_Array[20] = $time; // Assigned by system call
    D = 1.25; // Assign real time
end
```



wire vs. reg (1/2)

- Same "value" used both as 'wire' and as 'reg'

```
module dff (q, d, clk);  
    output reg q; // reg declaration,  
    input wire d, clk; // wire declarations, since module  
        inputs  
  
    always @(posedge clk) begin  
        q <= d;  
        // remember q is declared reg and  
        // d is declared wire  
    end  
endmodule
```



wire vs. reg (2/2)

- Same "value" used both as 'wire' and as 'reg'

```
module t_dff;
  wire q, clk; // now declared as wire
  reg d; // now declared as reg

  dff FF(q, d, clk); // why is d reg and q wire?
  clkgen myclk(clk);
  initial begin
    d = 0;
    #5 d = 1;
  end
endmodule
```



Signed vs. Unsigned

- Net types and **reg** variables unsigned by default
 - Have to declare them as signed if desired!

```
reg signed[7:0] signedreg;  
wire signed[3:0] signedwire;
```

- All bit-selects and part-selects are **unsigned**
 - `A[6]`, `B[5:2]`, etc.
- **integer**, **real**, **realtime** are signed
- System calls can force values to be signed or unsigned

```
reg [5:0] A = $unsigned(-4);  
reg signed [5:0] B = $signed(4'b1101);
```



Operators with Real Operands

Arithmetic

Unary +/-

+ - * / **

Relational

> >= < <= No others allowed!

Logical

! && || No bit-selects!

Equality

== != No part-selects!

Conditional

? :

Strings

- Strings are stored using properly sized registers

```
reg[12*8: 1] stringvar; // 12 character string
// string assignment
stringvar = "Hello World";
```

- Uses ASCII values
- Unused characters are filled with zeros
- Strings can be copied, compared, concatenated
- Most common use of strings is in testbenches



Memories (1/2)

- A memory is an array of n-bit registers

```
reg[15:0] mem_name [0:127]; //128 16-bit words  
reg array_2D [15:0] [0:127]; // 2D array of 1-bit regs
```

- Can only access full word of memory

```
mem_name[122] = 35; // assigns word  
mem_name[13][5] = 1; // illegal - works in simulation  
array_2D[122] = 35; // illegal - causes compiler error  
array_2D[13][5] = 1; // assigns bit
```

- Can use continuous assign to read bits

```
assign mem_val = mem[13]; // get word in slot 13  
assign out = mem_val[5]; // get bit in slot 5 of word  
assign dataout = mem[addr];  
assign databit = dataout[bitpos];
```



Example: Memory

```
module memory(output reg[7:0] out, input[7:0] in, addr,
              input wr, clk, rst);
    reg [7:0] mem [0:255]; // memory cells
    reg [8:0] raddr;      // for reset memory

    always @(posedge clk) begin // WRITE operation
        if(rst) begin // synchronous reset!
            for(raddr = 0; raddr < 256; raddr = raddr + 1)
                begin mem[raddr] <= 8'd0; end
            end
        else if (wr) begin
            mem[addr] <= in; // synchronous write
        end
    end

    always @(posedge clk) begin // READ operation
        out <= mem[addr]; // synchronous read
    end
endmodule
```



Control Statements

- Behavioral Verilog looks a lot like software
 - (risk! - danger and opportunity)
- Provides similar control structures
 - Not all of these actually synthesize, but some non-synthesizable statements are useful in **testbenches**
- What kinds synthesize?
 - **if**
 - **case**
 - **for** loops with constant bounds



if, else if, else

- Operator ? : for simple conditional assignments
- Sometimes need more complex behavior
- Can use **if-statement!**
 - Does not conditionally "execute" block of "code"
 - Does not conditionally create hardware!
 - It makes a **multiplexer** or similar logic
- Generally:
 - Hardware for all paths is created
 - All paths produce their results in parallel
 - One path's result is selected depending on the condition



Potential Issues With if

Can sometimes create long multiplexer chains

```
always @(select, a, b, c, d) begin
    out = d;
    if(select == 2'b00) out = a;
    if(select == 2'b01) out = b;
    if(select == 2'b10) out = c;
end
```

```
always @(a, b, c, d) begin
    if (a) begin
        if (b) begin
            if (c) out = d;
            else out = ~d;
        else out = 1;
    else out = 0;
end
```



if Statement: Flip-Flop Set/rst

```
module f_sr_behav(q, q_n, data, set, rst, clk);
    input data, set, clk, rst;
    output q, q_n;
    reg q;
    assign q_n= ~q; // continuous assignment

    /* Flip-flop with synchronous set/rst */
    always @(posedge clk) begin
        // Active-high set and rst
        if(rst) q <= 1'b0;
        else if(set) q <= 1'b1;
        else q <= data;
    end
endmodule
```

Does set or rst have priority?

case Statements

- Verilog has three types of case statements:
 - **case**, **casex**, and **casez**
- Performs bitwise match of expression and case item
 - Both must have same bitwidth to match!
- **case**
 - Can detect x and z! (only in simulation)
- **casez**
 - Can detect x(In simulation)
 - Uses z and ? as wildcard bits in case items and expression
- **casex**
 - Uses x, z, and ? as wildcard bits in case items and expression



Using `case` To detect `x` And `z`

- Only use this functionality in a testbench; it won't synthesize!
- Example taken from Verilog-2001 standard;
- Cannot be synthesized

```
case(sig)
  1'bz: $display("Signal is floating.");
  1'bx: $display("Signal is unknown.");
  default: $display("Signal is %b.", sig);
endcase
```



casex Statement

- Uses x, z, and ? as single-bit wildcards in case item and expression
- Uses only the first match encountered –Inherent **priority!**
- Treats x, z, and ? as don't care

```
always @(code) begin
    casex(code) // case expression
        2'b0?: control = 8'b00100110; //case item 1
        2'b10: control = 8'b11000010; //case item 2
        2'b11: control = 8'b00111101; //case item 3
    endcase
end
```

What is the output for code = 2'b01?

What is the output for code = 2'b1x?

casex construct is often used to describe logic with priority



casez Statement

- Uses z, and ? as single-bit wildcards in case item and expression
- Use z as don't care, x is a value
- Uses first match encountered

```
always @(code) begin
    casez(code)
        2'b0?: control = 8'b00100110; // item 1
        2'bz1: control = 8'b11000010; // item 2
        default: control = 8b'xxxxxxxx; // item 3
    endcase
end
```

Adding a default case statement is a great way to avoid inferring latches and make debugging easier!

What is the output for code = 2b'01?

What is the output for code = 2b'zz?



"Don't Care" Assignment With case

- Sometimes we know not all cases will occur
- Can "don't care" what is assigned

```
always @(state, b) begin
  case(state)                                // state is "expression"
    2'd0: next_state = 2'd1;                // 2'd0 is case item
    2'd1: next_state = 2'd2;                // ordering implied
    2'd2: if(b) next_state = 2'd0;
         else next_state = 2'd1;
    default: next_state = 2'dx;             // for all other states,
  endcase                                    // don't care what is
                                              // assigned
end
```



"Don't Care" Assignment With if

- Some combinations don't happen
- Can "don't care" what is assigned
 - For the real hardware, the actual value assigned is either 1 or 0 (or a vector of 1s and/or 0s), but the **synthesizer** gets to choose

```
always @(a, b, c) begin
    if(a && b)
        d = c;
    else if(a)
        d = ~c;
    else
        d = 1'bx;
end
```

For what inputs does the "don't care" value of d happen?



Inferring Latches

- Earlier we saw how to explicitly create latches
- We can also implicitly "infer" latches
 - Often this is unintentional and the result of poor coding, accidentally creating a latch instead of comb. logic
 - Unintentional latches are a leading cause of simulation and synthesis results not matching!
- Two common ways of inferring latches
 - Failing to fully specify all possible cases when using if/else, case, or conditional assignment when describing **combinational** logic
 - Failing to assign values to each variable in **all** cases



Unintended Latches [1] (BAD)

Always use else or provide “default value” when using if to describe combinational logic!

```
always @(en, a, b) begin
    if(en) c = a + b; // latch! - What about en= 1'b0?
end
```

```
always @(en, a, b) begin
    c = 8'b0;          // Fixed! Assign default value to C
    if(en) c = a + b; // Will be overwritten if en=1'b1
end
```

```
always @(en, a, b) begin
    if(en) c = a + b; // Fixed! Add an Else statement
    else c = 8'b0;    // Could have used a different value
end
```



Unintended Latches [2] (BAD)

Make sure that no matter what the value of your case selector is, if a variable is assigned in one case, it must be assigned in EVERY case.

```
always @(sel, a, b)
case(sel)
  2'b00 : begin
    out1 = a + b;
    out2 = a - b;
  end
  2'b01 : out1 = a + b; //Latch! What about out2's value?
  2'b10 : out2 = a - b; //Latch! What about out1's value?
  //Latch! What about out1 and out2's values for sel=2'b11?
endcase
```

How could we modify this code to remove the latches?



Mux With if...else if...else

What happens if we forget select in the trigger list?

What happens if select is 2'bxx?

```
module Mux_4_32_if (output [31:0] oData,  
                  input [31:0] iData3, iData2, iData1, iData0,  
                  input [1:0] select, input enable);  
    reg [31: 0] mux_out;  
    // add the enable functionality  
    assign oData = enable ? mux_out : 32'bz;  
    // choose between the four inputs  
    always @(iData3 or iData2 or iData1 or iData0 or select)  
        if      (select == 0) mux_out = iData0;  
        else if (select == 1) mux_out = iData1;  
        else if (select == 2) mux_out = iData2;  
        else      mux_out = iData3;  
endmodule
```



Mux With case

Case statement implies priority unless use parallel_case pragma

What happens if select is 2'bxx?

```
module Mux_4_32_if (output[31:0] oData,  
                  input[31:0] iData3, iData2, iData1, iData0,  
                  input[1:0] select, input enable);  
    reg[31: 0] mux_out;  
    // add the enable functionality  
    assign oData = enable ? mux_out : 32'bz;  
    // choose between the four inputs  
    always @(iData3 or iData2 or iData1 or iData0 or select)  
        case(select)  
            2'd0: mux_out = iData0;  
            2'd1: mux_out = iData1;  
            2'd2: mux_out = iData2;  
            2'd3: mux_out = iData3;  
        endcase  
endmodule
```



Encoder With if...else if...else

```
module encoder (output reg[2:0] Code,  
               input [7:0] Data);  
  
    always @(Data) begin // encode the data  
        if      (Data == 8'b00000001) Code = 3'd0;  
        else if (Data == 8'b00000010) Code = 3'd1;  
        else if (Data == 8'b00000100) Code = 3'd2;  
        else if (Data == 8'b00001000) Code = 3'd3;  
        else if (Data == 8'b00010000) Code = 3'd4;  
        else if (Data == 8'b00100000) Code = 3'd5;  
        else if (Data == 8'b01000000) Code = 3'd6;  
        else if (Data == 8'b10000000) Code = 3'd7;  
        else Code = 3'bxxx; //invalid, so don't care  
    end  
  
endmodule
```



Encoder With case

```
module encoder (output reg[2:0] Code, input [7:0] Data);  
  
    always @(Data) begin // encode the data  
        case(Data)  
            8'b00000001 : Code = 3'd0;  
            8'b00000010 : Code = 3'd1;  
            8'b00000100 : Code = 3'd2;  
            8'b00001000 : Code = 3'd3;  
            8'b00010000 : Code = 3'd4;  
            8'b00100000 : Code = 3'd5;  
            8'b01000000 : Code = 3'd6;  
            8'b10000000 : Code = 3'd7;  
            default : Code = 3'bxxx; // invalid, so don't care  
        endcase  
    end  
endmodule
```




Priority Encoder With casex

```
module priority_encoder (output reg[2:0] Code,
                        output valid_data,
                        input[7:0] Data);
    assign valid_data = |Data; // "reduction or" operator
    always @(Data) // encode the data
        casex(Data)
            8'b1xxxxxxx : Code = 7;
            8'b01xxxxxx : Code = 6;
            8'b001xxxxx : Code = 5;
            8'b0001xxxx : Code = 4;
            8'b00001xxx : Code = 3;
            8'b000001xx : Code = 2;
            8'b0000001x : Code = 1;
            8'b00000001 : Code = 0;
            default: Code = 3'bxxx; // should be at least one 1,
            don't care
        endcase
endmodule
```



Seven Segment Display

 

```
module Seven_Seg_Display(Display, BCD, Blanking);
    output reg[6: 0] Display;// abc_defg
    input[3: 0] BCD;
    input Blanking;
    parameter BLANK = 7'b111_1111; // active low
    parameter ZERO = 7'b000_0001; // h01
    parameter ONE = 7'b100_1111; // h4f
    parameter TWO = 7'b001_0010; // h12
    parameter THREE = 7'b000_0110; // h06
    parameter FOUR = 7'b100_1100; // h4c
    parameter FIVE = 7'b010_0100; // h24
    parameter SIX = 7'b010_0000; // h20
    parameter SEVEN = 7'b000_1111; // h0f
    parameter EIGHT = 7'b000_0000; // h00
    parameter NINE = 7'b000_0100; // h04
    always@ (BCD or Blanking)
        if (Blanking) Display = BLANK;
        else
            case (BCD)
                4'd0: Display = ZERO;
                4'd1: Display = ONE;
                4'd2: Display = TWO;
                4'd3: Display = THREE;
                4'd4: Display = FOUR;
                4'd5: Display = FIVE;
                4'd6: Display = SIX;
                4'd7: Display = SEVEN;
                4'd8: Display = EIGHT;
                4'd9: Display = NINE;
                default: Display = BLANK;
            endcase
endmodule
```



Ring Counter

```
module ring_counter (output reg[7: 0] count,  
                    input enable, clk, rst);  
  
    always @(posedge rst or posedge clk) begin  
        if (rst == 1'b1) begin count <= 8'b0000_0001; end  
        else if (enable == 1'b1)begin  
            case (count)  
                8'b0000_0001: count <= 8'b0000_0010;  
                8'b0000_0010: count <= 8'b0000_0100;  
                ...  
                8'b1000_0000: count <= 8'b0000_0001;  
                default: count <= 8'bxxxx_xxxx;  
            endcase  
        end  
    end  
endmodule
```



Ring Counter

```
module ring_counter (output reg[7: 0] count,  
                    input enable, clk, rst);  
  
    always @(posedge rst or posedge clk) begin  
        if (rst == 1'b1) begin // reset  
            count <= 8'b0000_0001;  
        end  
        else if(enable == 1'b1) begin // ring counter  
            count <= {count[6: 0], count[7]};  
        end  
    end  
end  
endmodule
```



Register With Parallel Load

```
module Par_load_reg4 (output reg [3: 0] Data_out,  
                    input [3: 0] Data_in,  
                    input load, clk, rst);  
  
    always @(posedge rst or posedge clk) begin  
        if(rst == 1'b1) begin //reset  
            Data_out <= 4'b0;  
        end  
        else if(load == 1'b1) begin // load  
            Data_out <= Data_in;  
        end  
        else begin // keep the same values  
            Data_out <= Data_out;  
        end  
    end  
end  
endmodule
```



Rotator

```
module rotator (output reg[7: 0] Data_out,  
               input[7: 0] Data_in,  
               input load, clk, rst);  
  
    always @(posedge rst or posedge clk) begin  
        if(rst == 1'b1) begin // reset  
            Data_out <= 8'b0;  
        end  
        else if(load == 1'b1) begin // load  
            Data_out <= Data_in;  
        end  
        else begin // rotate operation  
            Data_out <= {Data_out[6: 0], Data_out[7]};  
        end  
    end  
endmodule
```



Shift Register

```
module Shift_Reg(output reg[3: 0] oData, // out data
                 output oMSB, oLSB, // out MSB, LSB
                 input[3: 0] iData, input [1:0] sel,
                 input iMSB, iLSB, clk, rst);

    assign oMSB = oData[3];
    assign oLSB = oData[0];
    always @(posedge clk) begin
        if(rst) oData <= 0; // reset
        else case(sel) // select operation
            2'd0: oData <= oData; // Hold
            2'd1: oData <= {iMSB, oData[3:1]}; // Shift right
            2'd2: oData <= {oData[2: 0], iLSB}; // Shift left
            2'd3: oData <= iData; // Parallel Load
        endcase
    end
endmodule
```



Register File

Are the reads and writes synchronous or asynchronous?

```
module Register_File(output [15:0] oData1, oData2, // out
    input [15:0] iData, // data in
    input [2:0] rAddr1, rAddr2, wAddr, // read/write address
    input enWrite, clk); // write enable, clock

    // 16-bit by 8-word memory declaration
    reg [7:0] Reg_File [0:15];

    always @(posedge clk) begin
        if(enWrite) begin // WRITE operation
            Reg_File [wAddr] <= iData;
        end
        oData1 <= Reg_File[rAddr1]; // READ operation
        oData2 <= Reg_File[rAddr2]; // READ operation
    end
endmodule
```

